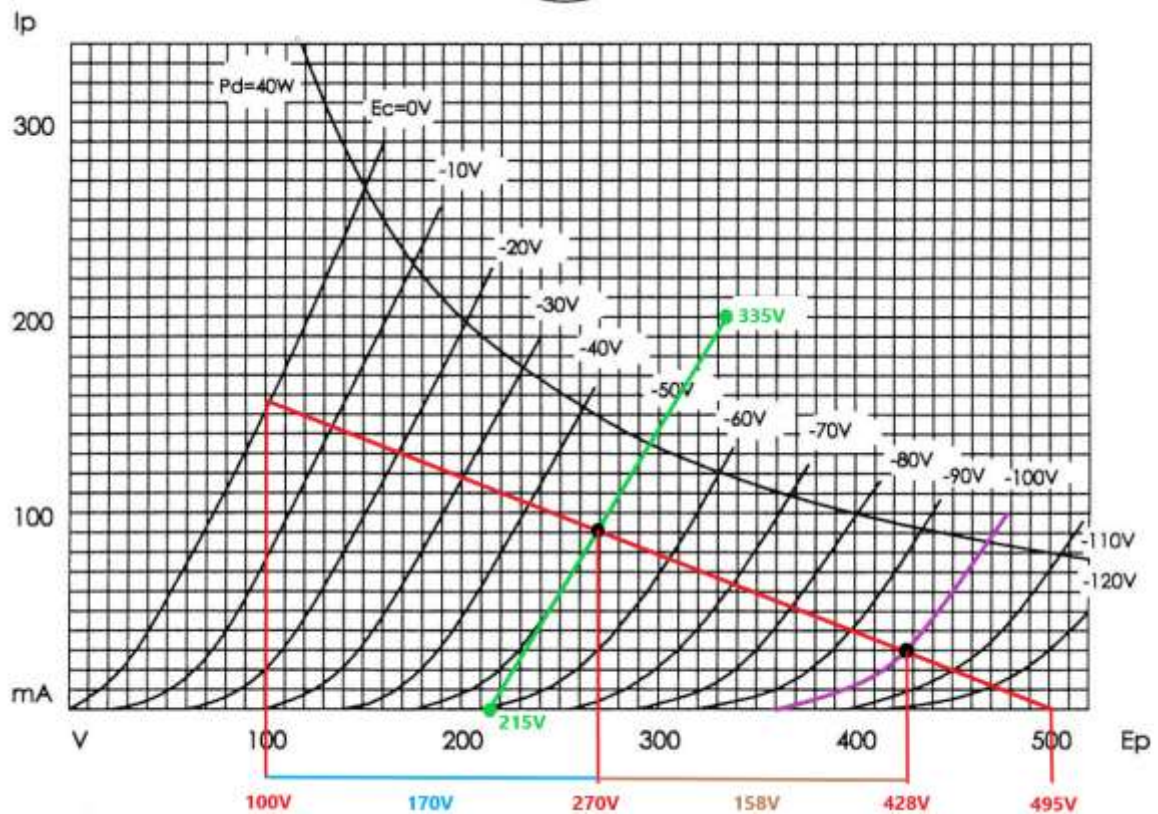


## Calculation of power Tube SE (Triode Mode)



Given:

**$B_+ = 270 \text{ V}$**

**Idle current ( $I_p$ ) Tube = 90mA.**

**Anode Dissipation:**

$$P_d = U * I = 270 \text{ V} * 90 \text{ mA} = 24,3 \text{ Watt}$$

This is within the limit,  **$P_{d(max)} = 40 \text{ Watt}$**

**Chosen Bias Current = 90 mA at 270V**

**$Z_a =$  Primary impedance of output transformer = 2,5 K $\Omega$**

A key characteristic of a transformer is that it can briefly store energy, allowing it to deliver a higher voltage than the supply voltage  **$B_+$** .

### Load line calculation:

$$U = I_p * Z_a = 90 \text{ mA} \times 2,5 \text{ K}\Omega = 225 \text{ V}$$

Draw a line from the **chosen idle current** to **Ec=0 V**.

Thus:

$$E_p = 270 \text{ V} + 225 \text{ V} = 495 \text{ V}$$

Starting at **495 V**, these two points define the slope of the load line.

We calculate the **usable power** because the full load line (due to curvature at the bottom of the graph) introduces too much distortion.

In this example, the maximum drive level is at **Ec = -100 V** (**purple line** with **black dot**), just above the curvature.

This corresponds to **50 V from the bias point Ec = -50 V**.

Extend another **50 V** to the other side from the bias point.

Here, this happens to reach **Ec = 0 V**, but this is not always the case.

With these three points, we can calculate the **usable power**.

### Usable Power Calculation:

$$P_{out} = \frac{1}{2} * \Delta V * \Delta I = \frac{1}{2} * 170 \text{ V} * (157 \text{ mA} - 90 \text{ mA}) = 5.6 \text{ Watt}$$

$$P_{out} = \frac{1}{2} * \Delta V * \Delta I = \frac{1}{2} * 158 \text{ V} * (90 \text{ mA} - 30 \text{ mA}) = 4,7 \text{ Watt}$$

The output power will therefore be approximately:

$$\frac{5,6 \text{ W} + 4,7 \text{ W}}{2} = 5,1 \text{ W per channel}$$

### **Distortion Calculation:**

You have a voltage of:

- 100V at Ec = 0V
- 270V at Ec = -50V
- 428V at Ec = -100V

$$E_p = 270 \text{ V} - 100 \text{ V} = 170 \text{ V}$$

$$E_p = 428 \text{ V} - 270 \text{ V} = 158 \text{ V}$$

$$THD_2 = \frac{1}{2} * \frac{170 \text{ V} - 158 \text{ V}}{170 \text{ V} + 158 \text{ V}} * 100 = 1,82\%$$

## Internal Resistance of the Tube:

$$R_i = \frac{V_a}{I_a} = \frac{335V - 215V}{200mA} = 600 \Omega$$